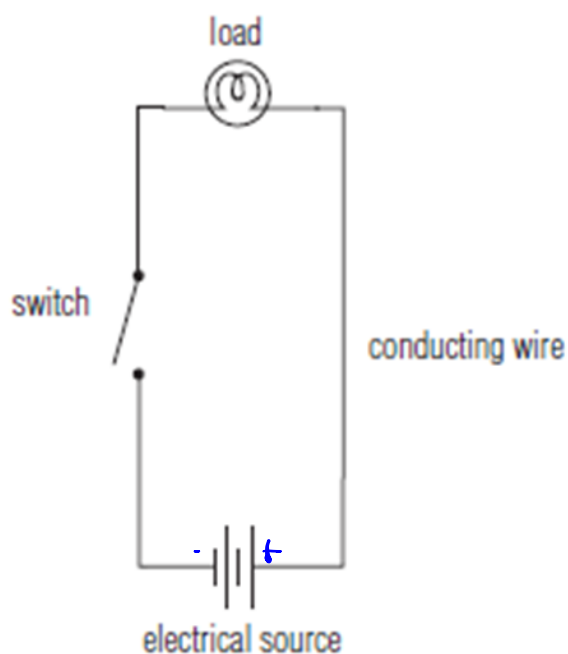


- What is the voltage drop of a circuit with a resistance of  $500\ \Omega$  that has a current of  $1.4\text{A}$  flowing through it.
- A  $3\text{-V}$  battery sends a current of  $0.10\text{A}$  through a light bulb. What is the resistance of the filament of the bulb?




$$\begin{array}{l} \triangle \\ \frac{V}{IR} \end{array} \quad \begin{array}{l} V = IR \\ = (1.4)(500) \\ = 700\text{V} \end{array} \quad \left| \quad \begin{array}{l} R = V \div I \\ = 3 \div 0.10 \\ = 30\ \Omega \end{array}$$



**Figure 11.26** The four basic parts of a circuit

**Figure 18**

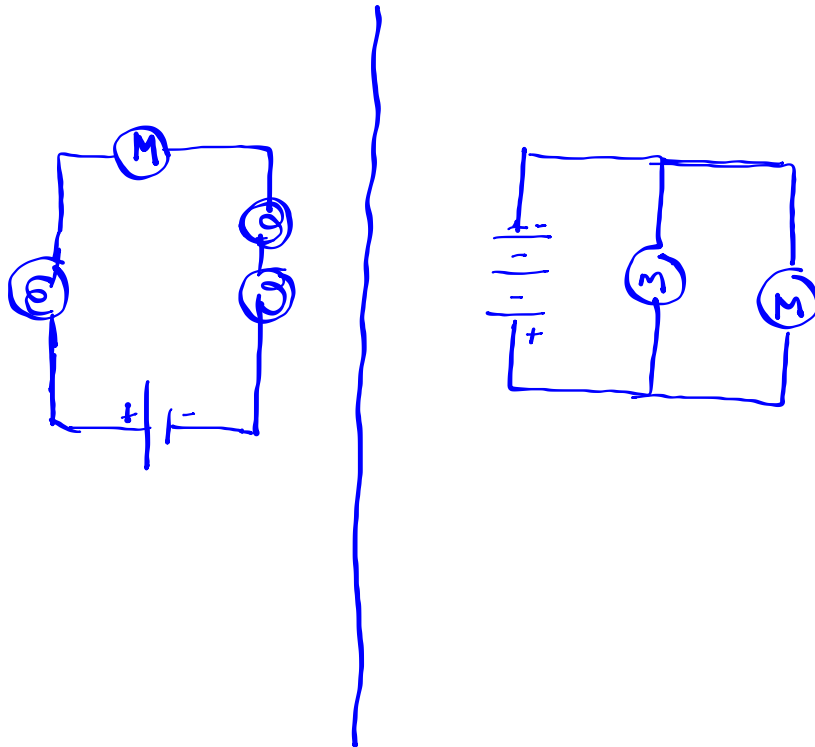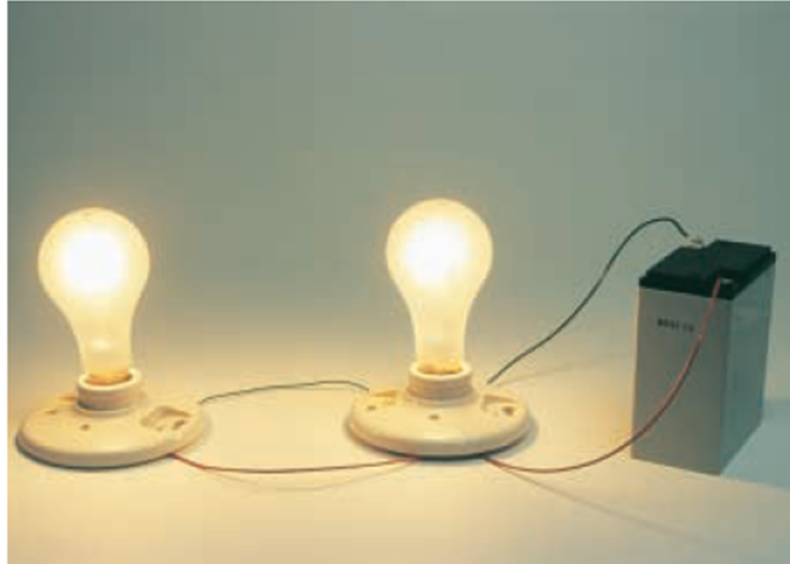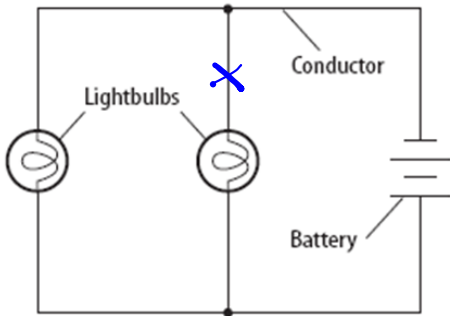In parallel circuits, the current follows more than one path. How will the voltage difference compare in each branch?



Test #	Bulb # →	1	2	3	4
Test #1		OFF	X	LIT	LIT
Test #2		X	OFF	LIT	LIT
Test #3		LIT	LIT	OFF	LIT
Test #4		X	OFF	OFF	X
Test #5		OFF	OFF	LIT	LIT
Test #6		X	X	X	OFF
Test #7		OFF	X	OFF	X

✓  
✓  
✓  
✓  
✓  
✓  
✓

